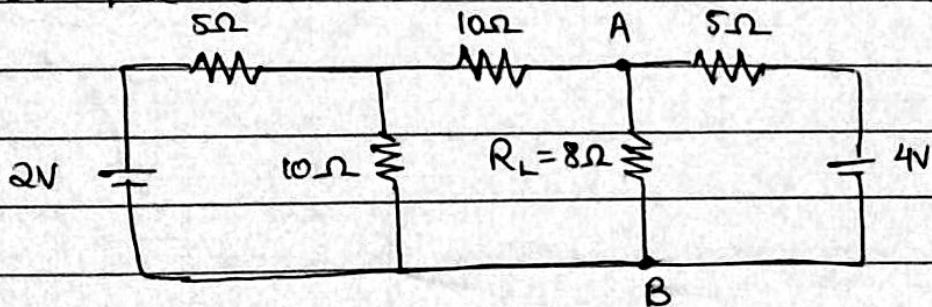


~~Objectives~~ Thévenin's theorem.


Steps to apply -

- ① Remove the branch resistance.
- ② Calculate the voltage across these open circuited terminals.
 $\therefore \text{find } V_{TH}$.
- ③ Replace all sources by their internal resistances to find R_{TH} .
- ④ Draw Thévenin's equivalent circuit showing source V_{TH} with resistance R_{TH} in series.
- ⑤ Reconnect the branch resistance.
 \therefore The required current through the branch is given by
 $I_L = \frac{V_{TH}}{R_L + R_{TH}}$

- ① 1.63 Determine the current through 8Ω resistor in the network.
 $\rightarrow \therefore$ The 8Ω resistor is the load resistor.



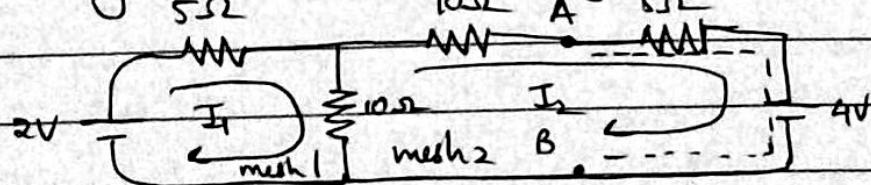Step 1: Removing resistance AB and finding $V_{AB} = V_{TH}$.



\therefore Applying KCL in mesh 1, $-2 + 5I_1 + 10(I_1 - I_2) = 0$.
 $\therefore 15I_1 - 10I_2 = 2$. ①

Now, Applying KCL to mesh 2, we get

$$10I_2 + 5I_3 + 4 + 10(I_2 - I_1) = 0.$$

$$10I_1 - 25I_2 = 4 \quad \textcircled{2}$$


Solving $\textcircled{1}$ and $\textcircled{2}$, $I_2 = -0.145\text{A}$.

$$\text{Hence } V_{AB} = 4 + 5(I_2) = 4 + 5(-0.145)$$

$$V_{TH} = 3.275\text{V.}$$

Now, for R_{TH} (Step 2)

$5\Omega, 10\Omega$ are in parallel.

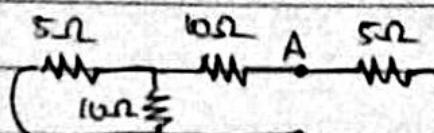

Their eq will be $10/3$ and it will be in series with 10Ω


and their eq will be 13.33Ω which will be then in parallel with 5Ω

$$\therefore R_{eq} = \frac{1}{1/13.33 + 1/5} \quad \therefore R_{TH} = R_{eq} = 3.636\Omega.$$


Step 3: Load current.

$$\text{we know, } I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{3.275}{8 + 3.636}$$
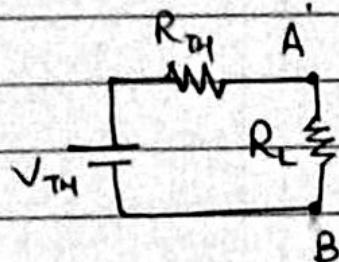
$$\therefore I_L = 0.281\text{ A} (\downarrow).$$




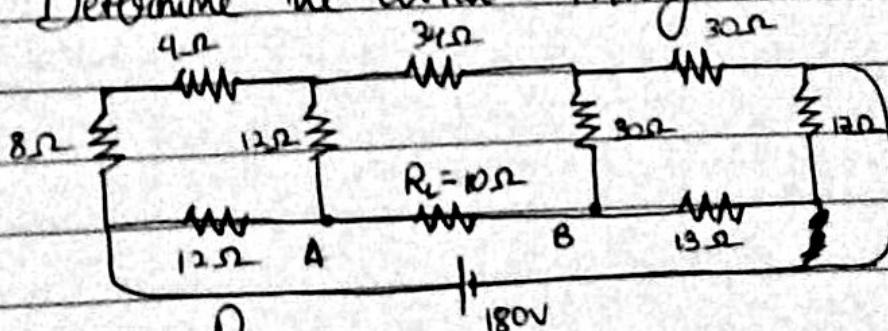② 1.64 Determine the current through 10Ω .



After removing R_L ,

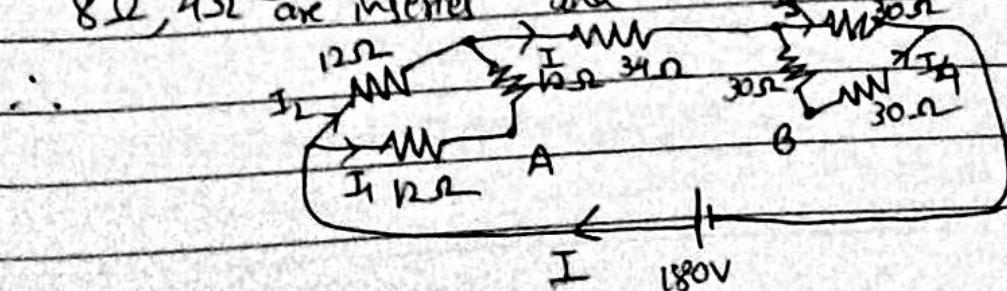$8\Omega, 4\Omega$ are in series and 13Ω and 12Ω are in series.



$$R_{eq} = 34 + \frac{1}{\frac{1}{12} + \frac{1}{14}} + \frac{1}{\frac{1}{30} + \frac{1}{60}} = 34 + \frac{8}{8} + \frac{20}{8} = 62 \Omega$$

$$\therefore I_{eq} = \frac{V}{R_{eq}} = \frac{180}{62} \quad I = I_1 + I_2 \quad (\text{from diagram})$$

$$\therefore I_1 = \frac{24}{36} \times I, \quad I_2 = \frac{12}{36} I$$

Similarly, $I = I_3 + I_4$


$$I_3 = \frac{60}{90} \times I, \quad I_4 = \frac{30}{90} \times I$$

$$\begin{aligned} \therefore V_{TH} &= V_{AB} = 12 \times I_2 + 34 \times I + 30 \times I_4 \\ &= 6 \times \frac{1}{3} I + 34 I + 30 \times \frac{1}{3} I \\ &= 48 I \\ &= \frac{180 \times 48}{62} \\ &= 31 \end{aligned}$$

$$\therefore V_{TH} = 139.35 V$$

Now, for R_{TH} .

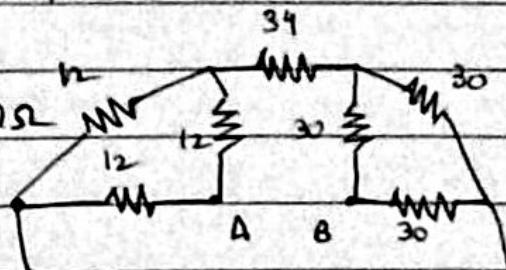Converting the 12Ω , 12Ω and 12Ω delta to star.



we get


$$R_1 = R_2 = R_3 = \frac{9 \times 12}{3 + 12} = 4 \Omega$$

$$\text{Similarly } R_4 = R_5 = R_6 = \frac{10}{3 + 30} = 10 \Omega$$

for 30Ω , 30Ω and 30Ω star delta to star.

\therefore New diagram will be
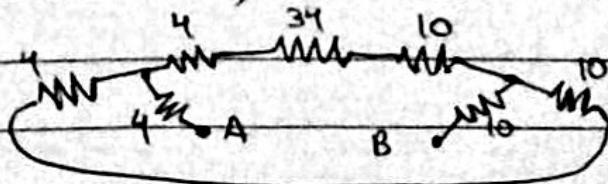
$$R_{eq} = 4 + 10 + \frac{1}{\frac{1}{14} + \frac{1}{48}}$$




$$R_{eq} = 24.84 \Omega = R_{TH}$$


\therefore Now we know,

$$I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{139.34}{10 + 24.84}$$
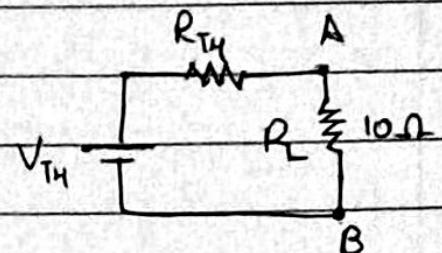
$$I_L = 4A (\rightarrow) = I_{10\Omega}$$



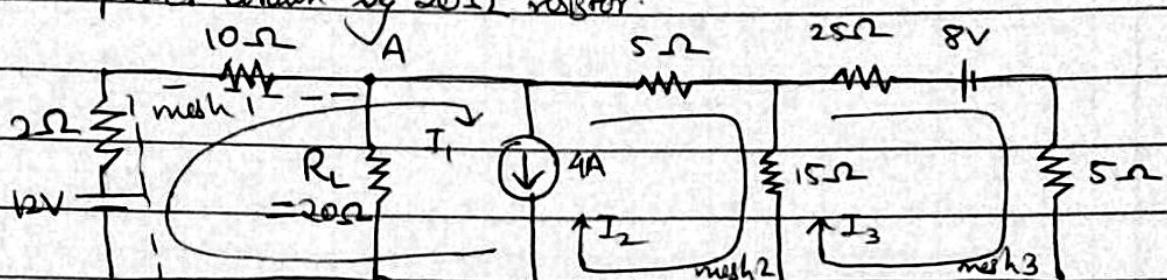- ③ 1.65 Obtain power drawn by 20Ω resistor.



$$\text{for power through } 20\Omega, P_{20\Omega} = I_{20\Omega}^2 R_{20\Omega}$$

$$= 20 I_{20\Omega}^2$$

Step 1: Calculation of V_{TH} .

$$\therefore I_1 - I_2 = 4 \quad \textcircled{1}$$

Mesh 1 and mesh 2 form a supermesh, Applying KVL

$$12 - 2(I_1) - 10(I_1) - 5(I_2) - 15(I_2 - I_3) = 0.$$

$$\therefore 12I_1 + 20I_2 - 15I_3 = 12 \quad \textcircled{2}.$$

Now, applying KVL to mesh 3,

$$-25(I_3) - 8 - 5(I_3) - 15(I_3 - I_2) = 0.$$

$$\therefore 15I_2 - 45I_3 = 8. \quad \textcircled{3}$$

$$\therefore \begin{bmatrix} 1 & -1 & 0 \\ 12 & 20 & -15 \\ 0 & 15 & -45 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 12 \\ 8 \end{bmatrix} \quad \text{from } \textcircled{1}, \textcircled{2} \text{ and } \textcircled{3}.$$

$$\Delta = 1 \left(20 \times 45 - 15 \times (-15) \right) + 1 \left(12 \times 45 \right) = -1215$$


$$= -15 \times 45 - 12 \times 45 \quad \therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{-3120}{-1215} = 2.57 A.$$

$$\Delta_1 = -27 \times 45 = -1215$$

$$\begin{aligned}\therefore V_{TH} &= V_{AB} \\ &= -10(I_1) - 2(I_1) + 12 \\ &= -12 \times 2.57 + 12 \\ V_{TH} &= -18.84V.\end{aligned}$$

Now,

Step II : Calculation of R_{TH} .

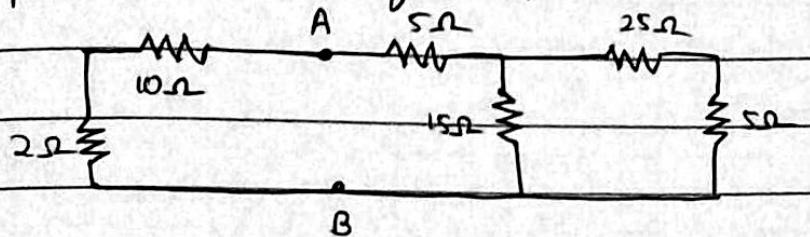


25Ω and 5Ω become 30Ω since they are in series. and then 30Ω and 15Ω act as a parallel connection whose equivalent resistance would be 10Ω .

10Ω and 5Ω will be in series and also 10Ω and 2Ω .

$\therefore 15\Omega$ and 12Ω will be in parallel as a result.

$$\therefore R_{TH} = R_{TH} = \frac{1}{\frac{1}{15} + \frac{1}{12}} = \frac{1}{Y_B \left(\frac{4+5}{20} \right)} = \frac{20}{3} = 6.67\Omega.$$

$$\therefore R_{TH} = 6.67\Omega.$$

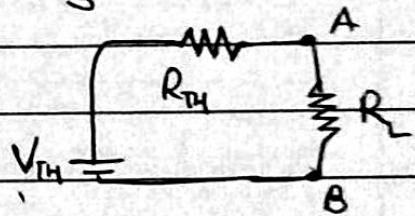


\therefore Step 3 : Calculation of load current.

$$I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{-18.84}{6.67 + 20} = 0.6706A (\uparrow).$$

$$\therefore I_{20\Omega} = 0.706A.$$

$$\begin{aligned}\therefore P_{20\Omega} &= 20 \times (0.706)^2 \\ &= 9.97W.\end{aligned}$$

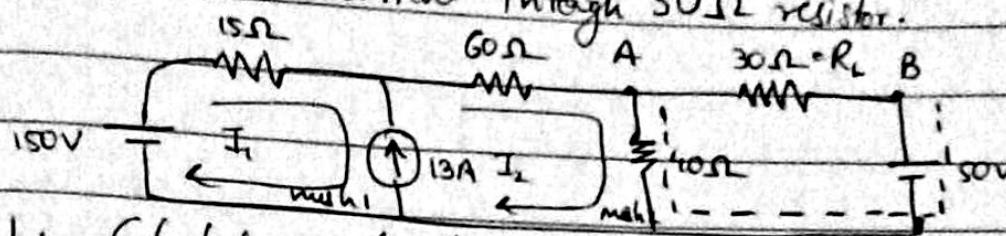④ 1.66 Determine current through 30Ω resistor.



Step 1: Calculation of V_{TH}

mesh 1 and 2 form a supermesh.
also $I_1 - I_2 = -13 \quad \text{--- (1)}$
 $\cdot I_1 = I_2 - 13$

Using KVL on supermesh,

$$150 - 15(I_1) - 60(I_2) - 40(I_2) = 0.$$

$$30 - 20I_2 - 3(I_2 - 13) = 0.$$

$$69 - 23I_2 = 0.$$

$$\therefore I_2 = 3A (\rightarrow) \therefore I_1 = -10A = (10A (\leftarrow))$$


$$\therefore V_{TH} = V_{AB}$$

$$= 50 - 40(I_2)$$

$$= 50 - 40 \times 3.$$

$$V_{TH} = -70V.$$

Step 2: Calculation of R_{TH}

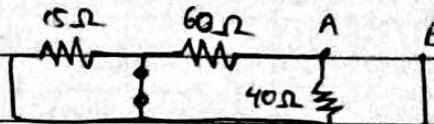


15Ω and 60Ω act as in ~~parallel~~ series.

$\therefore 75\Omega$ and 40Ω act as in parallel.

$$\therefore R_{TH} = \frac{1}{\frac{1}{75} + \frac{1}{40}} = 26.09\Omega.$$


$$\therefore R_{TH} = 26.09\Omega$$
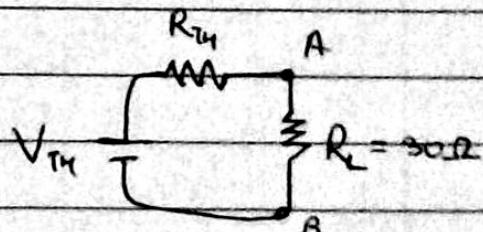
$$\text{Step 3. } I_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{70}{30 + 26.09} = 1.248A (\rightarrow)$$



\therefore The current through 30Ω resistor is $1.248A (\rightarrow)$

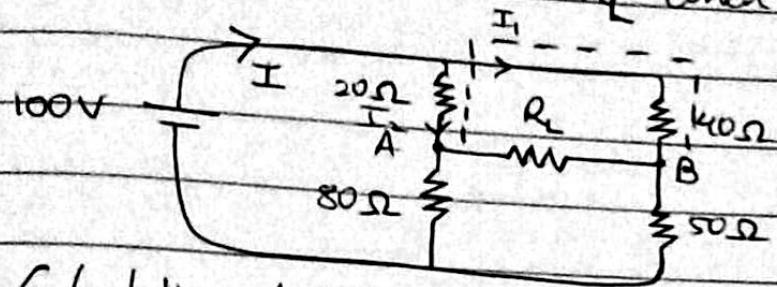(5) 1.67 Find the current in R_L when R_L takes values 5Ω , 10Ω and 20Ω .



Calculation of V_{TH}

$$\text{After removing } R_L, \quad I = I_1 + I_2$$

$$\therefore I_1 = \frac{80+20}{(80+20)+(40+50)} = \frac{100}{190} I.$$

$$\therefore I_2 = \frac{90}{190} I.$$

$$R_{eq} = \frac{1}{\frac{1}{190} + \frac{1}{100}} = \frac{190 \times 100}{190 + 100} = 47.37 \Omega.$$

~~$\therefore I = V/R = 100/47.37$~~

$$I = 2.11 A$$


$$\therefore I_2 = 1 A, \quad I_{11} = 1.11 A.$$

$$\begin{aligned} \therefore V_{TH} &= -20(I_2) + 40(I_1) \\ &= 20(2I_1 - I_2) \end{aligned}$$

$$V_{TH} = 24.44 V$$

Calculation of R_{TH}


~~40Ω~~ and 20Ω will be in parallel.

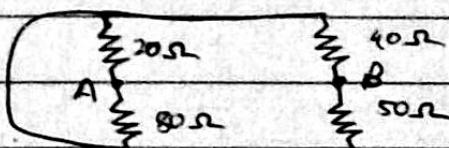

$$\therefore R_1 = \frac{1}{\frac{1}{20} + \frac{1}{80}} = 16. \quad 40\Omega \text{ and } 50\Omega \text{ will also be in parallel.}$$


$$R_2 = \frac{1}{\frac{1}{40} + \frac{1}{50}} = \cancel{22.22} \Omega. \quad A \xrightarrow{16\Omega} B$$
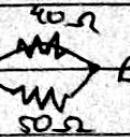
$$\therefore R_{TH} = R_{eq} = 16 + 22.22 = 38.22 \Omega.$$



Step 3: Calculation of load current.
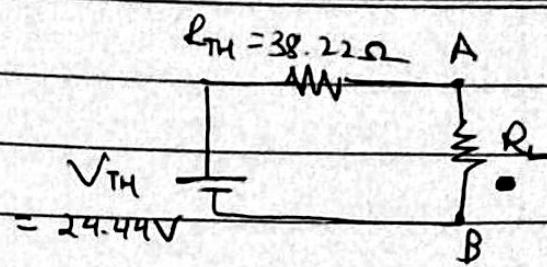
$$\therefore I_L = \frac{V_{TH}}{R_L + R_{TH}}$$




Hence,

$$\text{when } R_L = 5\Omega, I_L = \frac{24.44}{5+38.22} = 0.565A (\rightarrow)$$

$$R_L = 10\Omega, I_L = \frac{24.44}{10+38.22} = 0.507A (\rightarrow)$$

$$R_L = 20\Omega, I_L = \frac{24.44}{20+38.22} = 0.4198 (\rightarrow)$$

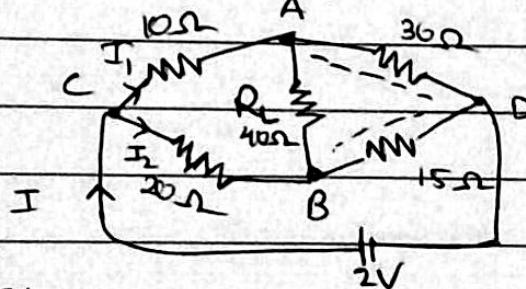- ⑥ 1.68 By Thévenin's theorem, find the current in 40Ω resistor.



Calculation of V_{TH} .

$$\text{After removing } R_L, R_{eq} = \frac{1}{\frac{1}{20+15} + \frac{1}{10+30}} = 18.67\Omega.$$

$$\therefore I = 0.107A, \quad \therefore I_1 = \frac{20+15}{20+15+10+30} \times I = \frac{7}{15}I$$

$$\therefore I_2 = \frac{10+30}{20+15+10+30} \times I = \frac{8}{15}I.$$


$$\therefore V_{TH} = V_{AB} = 30(I_1) - 15(I_2) = 15 \times \frac{1}{15}I (2 \times 7 - 8) = 6I.$$

$$V_{TH} = 0.642V$$


60

\therefore Calculation of R_m .

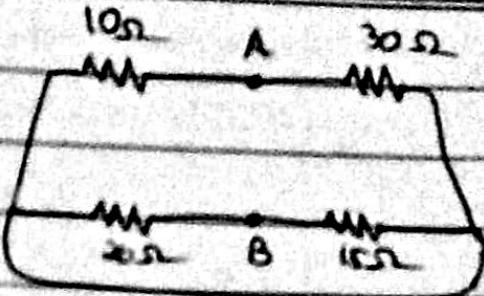$\therefore 10\Omega$ and 30Ω and
 20Ω and 15Ω would be
in parallel.


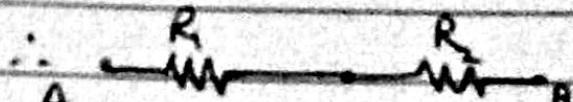
$$\therefore R_1 = \frac{1}{\frac{1}{10} + \frac{1}{30}} = 7.5\Omega$$



$$R_2 = \frac{1}{\frac{1}{20} + \frac{1}{15}} = 12\Omega$$

$$\therefore R_m = R_1 + R_2 = 16.07\Omega$$

\therefore Calculation of load current

$$I_L = \frac{V_m}{R + R_m}$$

$$= \frac{0.642}{40 + 16.07}$$

$$I_L = 0.01145A$$

$$\therefore I_L = 11.45mA (\downarrow)$$

