

SETSQUARE ACADEMY

Degree Engineering (Mumbai University)

F.E. Semester - I

Previous Year Paper Solutions

(December 2007 - May 2016)

Basic Electrical Engineering

Common for all Branches

Chapter 4 : TRANSFORMER

Theory Questions

- (1) What are assumptions (characteristics) for an Ideal Transformer? [D-13][4],[May 09][4],[May 08][3]

Solution:

Assumptions for an ideal transformer are:

- (i) There are no losses in the core
- (ii) No copper losses
- (iii) Leakage flux is assumed negligible. Therefore all the flux produced by the primary winding is coupled to the secondary.
- (iv) The primary and secondary winding resistances are negligible.
- (v) Voltage regulation is 0%.
- (vi) Efficiency is 100%.


- (2) Explain the principle of working for a single phase transformer and derive the e.m.f. equation for the same. [M-15][4],[D-14][6],[M-13][4],[D-12][4],[M-08][8]

Solution:

Working Principle of a Transformer.

A transformer is a static (or stationary) electrical apparatus by means of which electric power in one circuit is transformed into electric power of the same frequency in another circuit. It can raise or lower the voltage in a circuit but with a corresponding decrease or increase in current. The physical basis of a transformer is mutual induction between two coils linked by a common magnetic flux. In its simplest form it consists of two inductive coils which are electrically separated but magnetically linked through a path of low reluctance as shown in Fig. The two coils possess high mutual inductance. If one coil is connected to a source of alternating voltage, an alternating flux is set up in the laminated core, most of which is linked with the other coil in which it produces mutually induced emf (according to Faraday's Laws of Electromagnetic Induction

$|e_M| = M \frac{dI_1}{dt}$). If the second coil circuit is closed, using a load then a current flows in it and so electric energy is transferred (entirely magnetically) from the first coil to the second coil. The first coil, in which electric energy is fed from the a.c. supply, is called primary winding and the other from which energy is taken out, is called secondary winding.

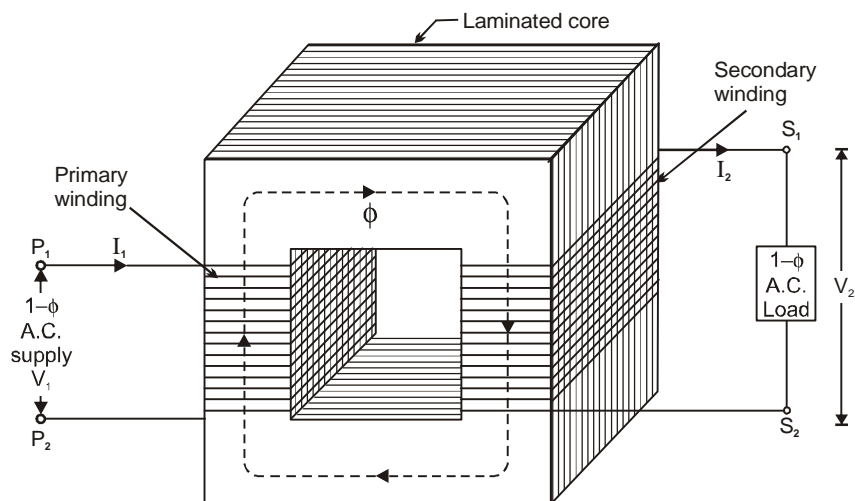


EMF Equation

Let N_1, I_1, R_1 and X_1 be the number of primary turns, primary current, primary resistance and primary leakage reactance respectively. Also let N_2, I_2, R_2 & X_2 be the corresponding secondary quantities.

Let V_1 & V_2 be the primary & secondary terminal voltages.

Further let E_1 & E_2 be the primary self induced emf & secondary mutually induced emf respectively.

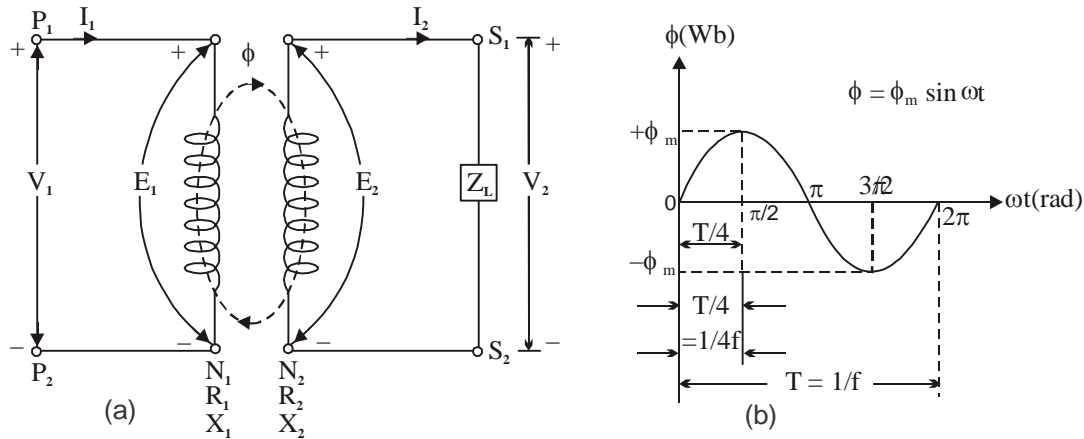Assumption: Though the flux ϕ varies sinusoidally, it is assumed that it varies uniformly i.e. linearly varies from the initial value of zero to the final value ϕ_m in the time $dt = T/4$.



From Fig. (b), clearly $d\phi = \phi_m$

The above flux links with the stationary primary turns N_1 during the time $dt = \frac{1}{4f}$.

\therefore As per Faraday's 2nd law of EMI, the magnitude of the average emf induced in the primary will be

$$E_{1av} = N_1 \frac{d\phi}{dt} = N_1 \frac{\phi_m}{1/4f} = 4f N_1 \phi_m$$

\therefore The rms value of the emf will be $E_1 = \text{Form Factor} \times E_{1av} = 1.11 \times 4f N_1 \phi_m$

(\because for a sinusoidally varying and alternating voltage, $\text{Form Factor} = \frac{\text{RMS value}}{\text{Average value}} = 1.11$)

$$\therefore E_1 = 4.44 f N_1 \phi_m \quad \text{.....(i)}$$

Similarly for secondary, we get $E_2 = 4.44 f N_2 \phi_m \quad \text{.....(ii)}$

Equations (i) and (ii) above are called emf equations of a transformer.

(3) What is the transformation ratio of an ideal transformer?

[Dec 07][2]

Solution:

For an ideal transformer, neglecting very small potential drops in the primary and secondary as the winding resistances are assumed zero

$$E_1 \approx V_1 \text{ and } V_2 \approx E_2$$

$$\therefore \frac{E_2}{E_1} = \frac{V_2}{V_1} = K$$

This ratio is known as the transformation ratio of an ideal transformer.

- (4) What are the losses in the transformer? Explain why the rating of transformer in KVA not in KW.

[M-14][4],[D-11][5],[D-10][5]

Solution:

Losses in a transformer

A transformer being static electrical apparatus, there are no friction or windage losses. Hence, the only losses occurring are:

Core or Iron Loss:

It includes both hysteresis loss and eddy current loss. Since the flux in the core remains almost constant for all loads, the core loss is constant.

Hysteresis loss, $W_h = \eta f B_m^{1.6} V$ watts;

Eddy current loss, $W_e = K_e f^2 t^2 B_m^2 V$ watts

Where, η = Hysterisis constant, f = frequency of the AC supply,
 B_m = max. flux density in the core, K_e = eddy current constant
 t = thickness of the core V = volume of the core material.

These losses are minimized by using steel of high silicon content for the core and by using very thin laminations, which are interleaved to reduce the air gap. Iron or core loss is found from the O.C. test.

Copper loss:

This loss is due to the ohmic resistance of the transformer windings.

$$\text{Total Cu loss} = (I_1^2 R_1 + I_2^2 R_2) = I_1^2 R_{01} = I_2^2 R_{02}$$

Cu loss is proportional to (current)² and hence (kVA)². Copper losses are found from S.C. test.

Rating of Transformer in KVA and not in KW

The rated transformer output is limited by heating and hence losses in the transformer, i.e. copper loss and iron loss. These losses depend upon the voltage and current, and are almost unaffected by the power factor of the load. Therefore transformer rated output is expressed in KVA and not in KW.

- (5) Derive condition for maximum efficiency of a transformer. Also derive equation for load at maximum efficiency.

[D-13][8]

Solution:-

Condition for maximum Efficiency :

$$\eta = \frac{\text{ouput power}}{\text{input power}} = \frac{\text{Input power} - \text{losses}}{\text{input power}}$$

Let copper loss; $W_{cu} = I_1^2 R_{01}$ or $W_{Cu} = I_2^2 R_{02}$

Iron(core) loss = W_i

Input power = $V_1 I_1 \cos \phi$

$$\text{So, } \eta = \frac{V_1 I_1 \cos \phi - I_1^2 R_{01} - W_i}{V_1 I_1 \cos \phi} = 1 - \frac{I_1 R_{01}}{V_1 \cos \phi} - \frac{W_i}{V_1 I_1 \cos \phi}$$

$$\text{for } \eta_{\max}, \frac{d\eta}{dI_1} = 0 \Rightarrow \frac{d\eta}{dI_1} = 0 - \frac{R_{01}}{V_1 \cos \phi} + \frac{W_i}{V_1 I_1^2 \cos \phi} = 0 \Rightarrow \frac{W_i}{V_1 I_1^2 \cos \phi} = \frac{R_{01}}{V_1 \cos \phi}$$

$$\therefore W_i = I_1^2 R_{01} \text{ or } W_i = I_2^2 R_{02}$$

Thus, the condition to achieve maximum efficiency is Iron loss = Copper loss

Load at η_{\max} :

Let at 'X' times full load, the efficiency is max.

So copper loss at η_{\max} , $= X^2 \times [W_{cu}]_{FL}$

But at η_{\max} , iron (or core) loss = copper loss

$$W_i = X^2 [W_{cu}]_{FL} \Rightarrow X = \sqrt{\frac{W_i}{[W_{cu}]_{FL}}}$$

$$\% \eta_{\max} = \frac{X \times \text{fullload KVA} \times \text{pf}}{(X \times \text{fullload KVA} \times \text{pf}) + 2 W_i} \times 100$$

\therefore load corresponding to maximum efficiency

$$[kVA]_{\max} = \left(\sqrt{\frac{W_i}{(W_{cu})_{FL}}} \right) \times (kVA)_{FL}$$

- (6) Draw the phasor diagram of a transformer on no load and explain the various currents and voltages in it.


[May 15][4],[May 15][6],[Dec 09][4]

Solution:

Phasor diagram of an ideal transformer with no load

An ideal transformer is one which has no iron and copper losses.

When the sinusoidally varying alternating supply voltage V_1 is applied across the primary, the sinusoidally varying alternating magnetising current I_μ starts flowing through primary, setting up flux ϕ (which is also sinusoidally varying and alternating) in the core. Since the primary coil is highly inductive, I_μ lags V_1 by 90° . We also know that the flux ϕ is in phase with I_μ ($\because \phi \propto I$).

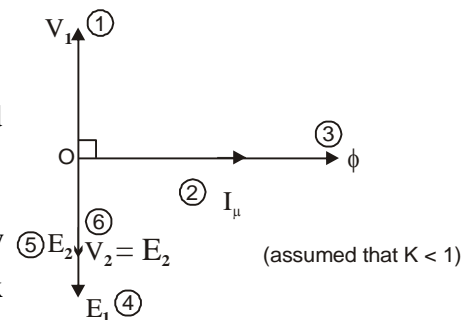

An emf E_1 is induced in the primary according to Faraday's first law of EMI and is called as primary emf of self inductance. It is in phase opposition to V_1 according to Lenz's law i.e. $E_1 \approx -V_1$.

As secondary is in the vicinity of primary, an emf of mutual inductance i.e. E_2 is induced in secondary which is in phase opposition to the very cause producing it i.e. V_1 and finally we get at the secondary terminals, the terminal voltage V_2 which is also opposite to the very cause producing it i.e. V_1 .

Thus we find that E_1 , E_2 and V_2 are in phase with each other and they are in phase opposition to V_1 i.e. the very cause producing them.

Phasor diagram of a practical transformer with no load


In a practical transformer with no load, the losses are

- (a) Magnetic losses in the core and
- (b) Very very small copper losses in the primary winding.

Now the no load current I_0 will be drawn from supply. It will consist of two components.

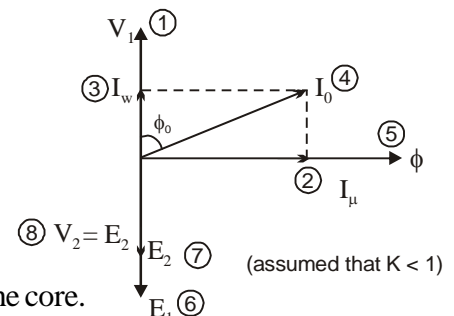- (i) The magnetising component I_μ responsible for setting up flux in the core.

It is lagging V_1 by 90° since the primary coil is highly inductive.



(ii) The loss component I_w which is responsible mainly for the iron loss and very small primary Cu loss. It is in phase with V_1 . This component is also called as active, working or iron loss component.

Usually I_0 is kept very small as compared to full load primary current I_{FL} so as to have higher efficiency of the transformer. I_{00} is comparatively larger than I_w .



E_2 is the emf induced in the secondary due to mutual induction while $V_2 = E_2$ is the terminal voltage across the secondary.

- (7) Draw phasor diagram of single phase transformer on resistive load [Unity power factor] and inductive load [lagging power factor]. [M-14][6],[D-12][6]

Solution:

Case I: Resistive load i.e. upf.

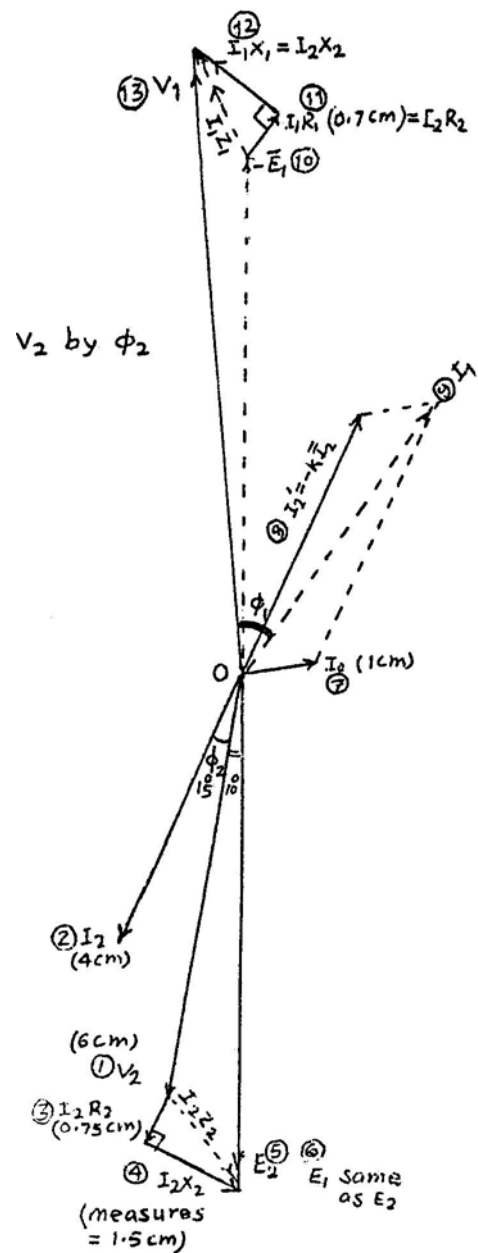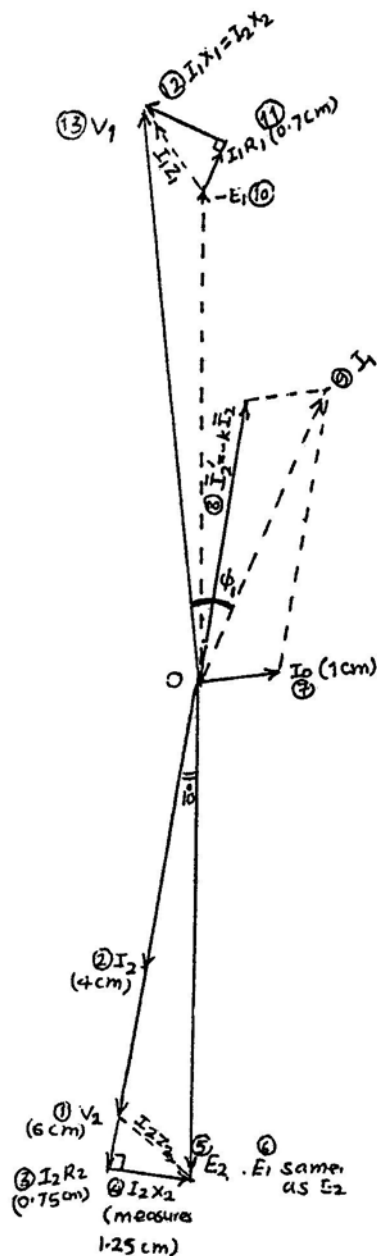Case II: Inductive load i.e. lagging p.f.



Note: It is observed that $E_2 > V_2$ for u.p.f & lagging p.f.

- (II) In Fig. (b) below is shown the circuit of a transformer in which the resistances and reactance are shown external to the windings

$R_0 = \frac{E_1}{I_w}$ is called excitation resistance which is responsible for no load losses.

$X_0 = \frac{E_1}{I_\mu}$ is called excitation reactance which is responsible for setting up the flux in the core.

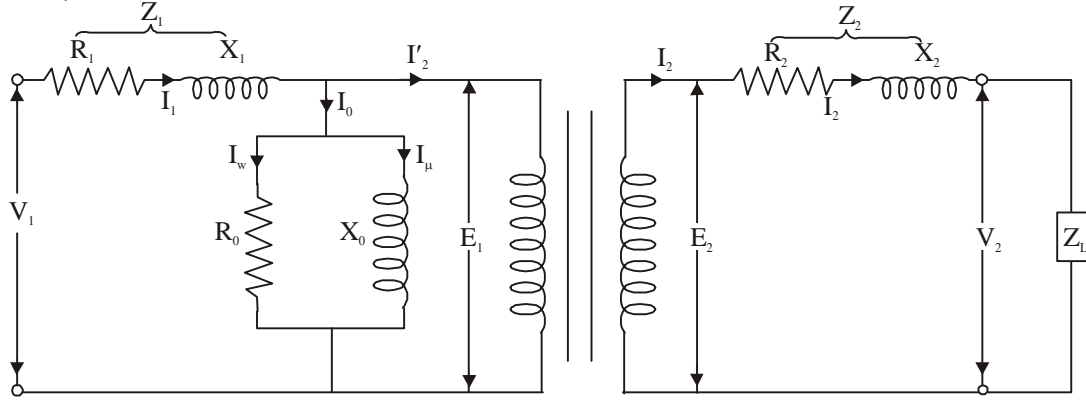


Fig. (b)

- (III) Transferring the secondary quantities on the primary side, we get following circuit as shown in Fig. (c) below

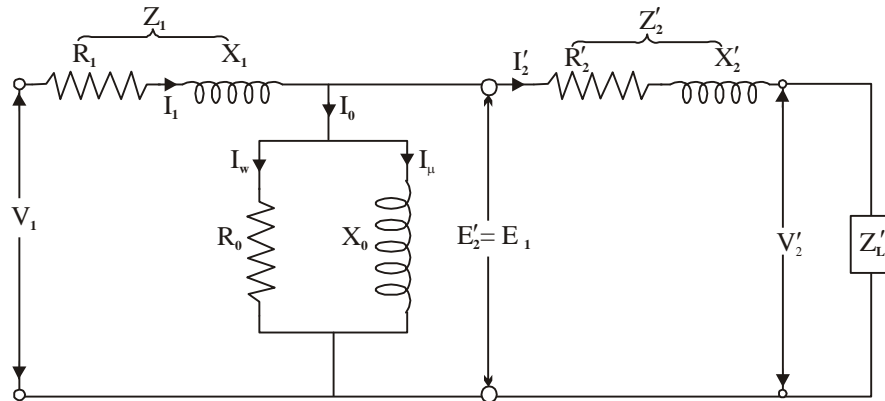


Fig. (c)

- (IV) $\because I_0$ is very small compared to the full load primary current I_{1FL} \therefore neglecting very small $I_0 R_1$ and $I_0 X_1$ potential drops i.e. assuming that $E_1 \simeq V_1$, we can transfer the parallel combination of R_0 and X_0 on the extrem left ie directly across V_1 \therefore We get following circuit as shown in Fig. (d) below :

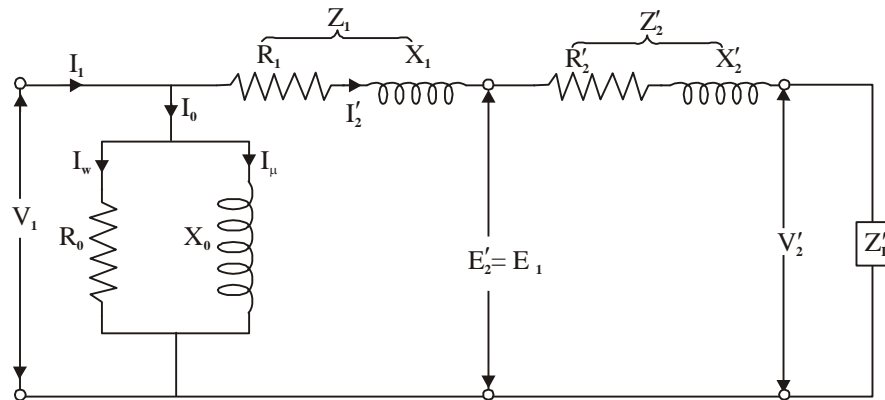


Fig. (d)

- (V) Finally, we get the following simplified circuit of the transformer as referred to primary shown in Fig. (e), where $R_{01} = (R_1 + R'_2)$ and $X_{01} = (X_1 + X'_2)$

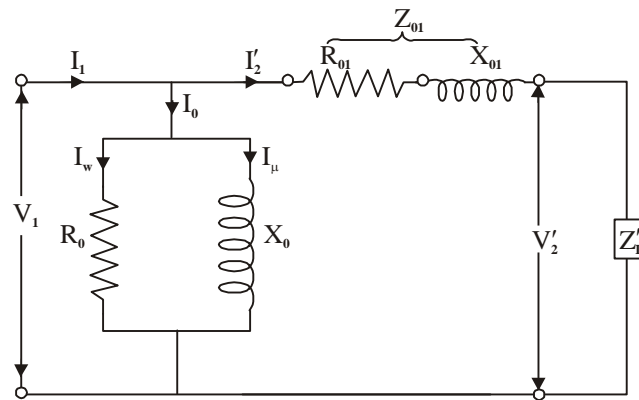


Fig. (e)

Voltage Regulation of a transformer:

- (i) The terminal voltage across the load is $\overline{V_2} = \overline{E_2} - \overline{I_2 Z_2}$.
Clearly, at no load, $I_2 = 0 \therefore V_2 = E_2$ and is the highest, however, as I_2 increases, $I_2 Z_2$ drop increases and therefore V_2 decreases. Voltage regulation takes care of this drop in the terminal voltages as load changes.
- (ii) General mathematical expression of voltage regulation.

$$\% \text{ Voltage Regulation} = \frac{V_{2NL} - V_{2L}}{V_{2NL}} \times 100 = \frac{E_2 - V_{2L}}{E_2} \times 100$$
- (iii) Like efficiency, voltage regulation is also specified at two factors viz load and the load p.f.
- (iv) Ideally the voltage regulation should be zero. However, for upf and lagging pf, depending upon the load, it varies between +2% to +5%, while for a leading pf it varies between -1% to -3%.
- (v) As mentioned above, regulation for upf and lagging pf is positive $\therefore E_2 > V_2$ however for leading pf it is negative $\therefore E_2 < V_2$


(10) With the help of a neat diagram explain how short circuit test is conducted on a single phase transformer
[M-15][6],[May-11][6]

Solution:

Short Circuit or Impedance test

Procedure:

The connections are made as shown in circuit diagram. Either of the sides HV or LV whichever is convenient (but preferably LV) is solidly short circuited and meters are connected to the other side. The supply is given through a continuously variable auto-transformer and the voltage is carefully and gradually increased till full load rated current flows through the short circuited winding and hence as well as through the metering side. It is generally observed that 5 to 10% the rated voltage is required to circulate the full load or rated current through the windings. Now the readings of the instruments are noted.

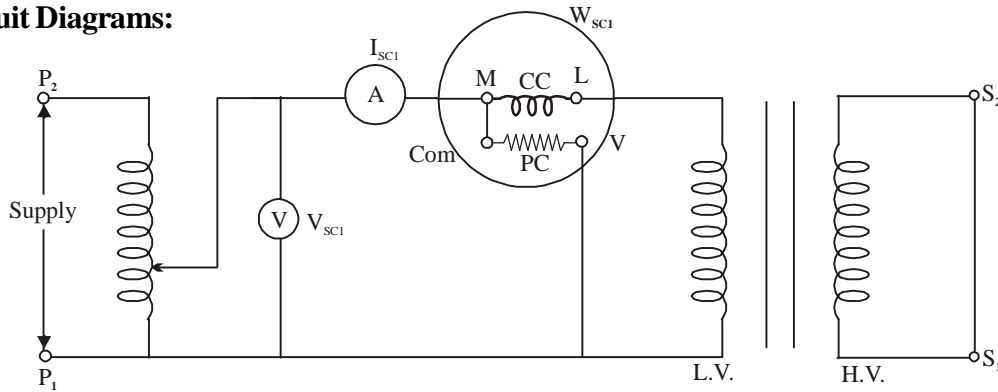Circuit Diagrams:

Note that here the transformer we have considered is of step-down type for the sake of convenience only & \therefore secondary is LV. it is shorted & meters are connected on primary here i.e. here short circuit test metering side (abbreviated as SCTMS) is primary.

Theory and Explanation:

As mentioned above since one of the sides is short circuited, it offers the least impedance to the current flow. \therefore it is seen that very small voltage of about 5 to 10% is required to be applied on the other side (i.e. metering side) for circulating the rated current. And the wattmeter reading indicates copper losses. This can be explained as follows.

As the applied voltage is very less, it is clear that the flux set up is also less since $V_1 = 4.44 f N_1 \phi_m$. $\therefore \phi_m \propto V_1$ and therefore B_m is also very less. Thus the iron losses can be neglected.

$\therefore W_h \propto B_m^{1.6}$. and $W_e \propto B_m^2$ will be very small.

The current flowing through the short circuited winding and hence through the metering side is the rated or full load current and therefore the wattmeter represents copper losses, W_{CuFL} .

Thus, from these two reasons we can say that the wattmeter reading during short circuit or impedance test represents copper loss.

Calculations :

Assuming here that, the metering side is primary, for the sake of convenience only, following calculations are made:

$$(i) \quad Z_{01} = \frac{V_{SC1}}{I_{SC1}}; \text{ Thus } Z_{01} \text{ can be calculated.}$$

$$(ii) \quad W_{SC1} = I_{SC1}^2 R_{01} \Rightarrow R_{01} = \frac{W_{SC1}}{I_{SC1}^2} \text{ and can be calculated.}$$

$$(iii) \quad \therefore X_{01} = \sqrt{(Z_{01})^2 - (R_{01})^2} \text{ is known.}$$

However, if the metering side is secondary, then we can modify the above calculations as:

$$(i) \quad Z_{02} = \frac{V_{SC2}}{I_{SC2}}, \text{ Thus } Z_{02} \text{ can be calculated.}$$

$$(ii) \quad W_{SC2} = I_{SC2}^2 R_{02} \Rightarrow R_{02} = \frac{W_{SC2}}{I_{SC2}^2} \text{ and can be calculated}$$

$$(iii) \quad X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} \text{ is known.}$$

(11) With the help of a neat diagram explain how open circuit test is conducted on a single phase transformer. [D-14][6],[M-11][6]


Solution:

Open Circuit or no load test:

Procedure:

In this test, either of the sides HV or LV of the transformer, whichever is convenient, is left open (but usually HV) and rated supply voltage at the normal frequency is applied to the other side. Ammeter, voltmeter and wattmeter are connected on this side, the readings of which are carefully noted.

Circuit Diagram:

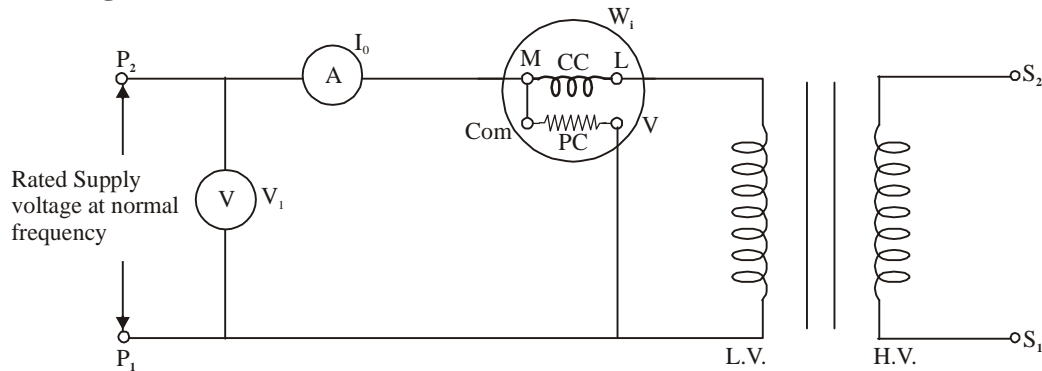

Note that here the transformer we have considered is of step up type for the sake of convenience only & \therefore primary is LV, meters are connected on primary i.e. here open circuit test metering side (abbreviated as OCTMS) is primary.

Theory and Explanation

In a transformer the main losses are:

Constant iron losses (W_i) consisting of

- (a) Hysteresis losses, $W_h = \eta f B_m^{1.6} V$ watts (b) Eddy current losses $W_e = K_e f^2 t^2 B_m^2 V$ watts

Variable copper losses in primary ($I_1^2 R_1$) and secondary ($I_2^2 R_2$)

When the transformer is on no load, the current drawn from the supply by the transformer is called “No load current” I_0 and is very small. And the wattmeter reading indicates constant iron losses W_i during the test.

Calculations:

Assuming that primary is LV here, i.e. metering side is primary for the sake of convenience only, following calculations are made:

- (i) Wattmeter reading say $W_i = V_1 I_0 \cos \phi_0$
 Since W_i , V_1 and I_0 can be read from the respective instruments, the no load power factor
 $\cos \phi_0 = \frac{W_i}{V_1 I_0}$ can easily be determined.
- (ii) $\therefore I_\mu = I_0 \sin \phi_0$ and $I_w = I_0 \cos \phi_0$ can now be determined.
- (iii) $\therefore X_0 = \frac{V_1}{I_\mu}$ & $R_0 = \frac{V_1}{I_w}$ can also be found out. [Note that $R_0 > X_0 \therefore I_w < I_\mu$]

However, if the metering side is secondary then we can modify the above calculations as:

- (i) $W_i = V_2 I'_0 \cos \phi'_0$ $\therefore \cos \phi'_0$ and $\sin \phi'_0$ can be found
- (ii) $I'_\mu = I'_0 \sin \phi'_0$ and $I'_w = I'_0 \cos \phi'_0$ can now be determined
- (iii) $X'_0 = \frac{V_2}{I'_\mu}$ and $R'_0 = \frac{V_2}{I'_w}$ are found.

Numerical Problems

Type I : Basic Sums

- (1) A 5 kVA, 240/2400 V, 50 Hz single phase transformer has the maximum value of flux density as 1.2 Tesla. If the e.m.f. per turn is 8 V. Calculate the number of primary and secondary turns and the primary and secondary current at full load. [D-14][4]

Solution:-

$$E_1 = 4.44 f \phi_m N_1 \quad \therefore N_1 = \frac{E_1}{4.44 f \phi_m} = \frac{240}{4.44 \times 50 \times 1.2} = 0.9 \cong 1$$

$$E_2 = 4.44 f \phi_m N_2 \quad \therefore N_2 = \frac{E_2}{4.44 f \phi_m} = \frac{2400}{4.44 \times 50 \times 1.2} = 9.009 \cong 9$$

$$I_{1FL} = \frac{\text{KVA rating}}{V_1} = \frac{5\text{KVA}}{240} = 20.833\text{A}$$

$$I_{2FL} = \frac{\text{KVA rating}}{E_2} = \frac{5000\text{VA}}{2400} = 2.083\text{A}$$

- (2) A 3000/200 V, 50 Hz single phase transformer has a cross sectional area of 150 cm² for the core. If the number of turns on the low voltage winding is 80, determine number of turns on the high voltage winding and maximum value of flux density in the core. [M-13][6]

Solution:-

$$\text{Given: } E_1 = 3000\text{V}, \quad f = 50\text{Hz}, \quad E_2 = 200\text{V}, \quad N_2 = 80\text{turns}, \quad A = 150\text{cm}^2$$

$$\text{To find: } N_1 = ? \quad B_m = ?$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} \Rightarrow N_1 = N_2 \times \frac{E_1}{E_2} = 80 \times \frac{3000}{200} = 1200$$

$$\therefore E_1 = 4.44 f \phi_m N_1 = 4.44 f B_m A N_1 = 4.44 \times 50 \times B_m \times 150 \times 10^{-4} \times 1200$$

$$\therefore B_m = \frac{3000}{4.44 \times 50 \times 150 \times 10^{-4} \times 1200} = 0.75 \text{ Weber / m}^2 = 0.75\text{T}$$

- (3) A 50 KVA, 2200/440V, 50 Hz single phase transformer has primary turns of 200. [May 12][5]
Determine: (i) flux in core (ii) Secondary turns (iii) rated primary current (iv) rated secondary current

Solution:

$$\text{Given: } \text{kVA} = 50, \quad V_1 = 2200 \text{ V}, \quad V_2 = 440 \text{ V}, \quad f = 50 \text{ Hz}, \quad N_1 = 200$$

$$1. \text{ Flux in core: } V_1 = 4.44 f N_1 \phi_m \Rightarrow 2200 = 4.44 \times 50 \times 200 \times \phi_m \Rightarrow \phi_m = 0.04954 \text{ Wb}$$

$$2. \text{ Secondary turn: } N_2 = \frac{V_2}{V_1} \times N_1 = \frac{440}{2200} \times 200 = 36.36$$

$$3. \text{ Rated Primary current: } I_1 \text{ rated} = \frac{\text{kVA} \times 10^3}{V_1} = \frac{50 \times 10^3}{2200} = 22.73 \text{ Amp.}$$

$$4. \text{ Rated Secondary current: } I_2 \text{ rated} = \frac{\text{kVA} \times 10^3}{V_2} = \frac{50 \times 10^3}{440} = 113.64 \text{ Amp.}$$

Type II : O.C., S.C., Efficiency and Regulation of a Transformer

- (1) A 5kVA, 1000/200V, 50 Hz, single phase transformer gave the following test results.

O.C. test (hv. side) : 1000V 0.24 A 90 W

S.C. test (hv. side) : 50V 5A 110 W

Calculate the equivalent circuit parameters of the transformer and draw the equivalent circuit diagram.

[M-16][8],[D-15][6],[M-15][8]

Solution:-

5 KVA, 1000/200 V, 50 Hz

Open circuit Test: $V_1 = 1000\text{ V}$, $I_0 = 0.24\text{ A}$, $W_0 = 90\text{ W}$

$$\cos \phi_0 = \frac{W_0}{V_1 I_0} = 0.375 \quad \therefore \quad \phi_0 = 67.98^\circ; \sin \phi_0 = 0.927$$

$$R_0 = \frac{V_1}{I_0 \cos \phi_0} = \frac{1000}{0.24 \times 0.375} = 11.1111\text{ k}\Omega$$

$$X_0 = \frac{V_1}{I_0 \sin \phi_0} = \frac{1000}{0.24 \times 0.927} = 4.4948\text{ k}\Omega$$


$$\text{Short circuit Test: } W = I_1^2 \cdot R_{ol} \Rightarrow 110 = 5^2 \times R_{ol}$$

$$\therefore R_{ol} = 4.4\Omega$$

$$Z_{ol} = \frac{V_{sc}}{I_1} = \frac{50}{5} = 10\Omega$$

$$X_{ol} = \sqrt{Z_{ol}^2 - R_{ol}^2} = \sqrt{10^2 - 4.4^2} = 8.98\Omega$$

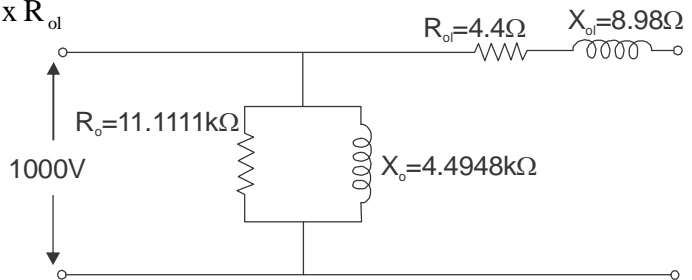Equivalent circuit reference to primary side of transformer is shown in fig.



- (2) A 30 kVA, 2400/120V, 50Hz transformer has high-voltage winding resistance of 0.1Ω and leakage reactance of 0.22Ω . The low voltage winding resistance is 0.035Ω and leakage reactance is 0.012Ω . Calculate equivalent resistance as referred to primary and secondary, equivalent reactance as referred to primary and secondary, equivalent impedance as referred to primary and secondary. Copper loss at full load and at 75% of full load.
- [D-14][8],[M-13][8][D-12][8]

Solution:-

$$E_1 = 2400\text{ V}, \quad E_2 = 120\text{ V}, \quad R_1 = 0.1\Omega, \quad R_2 = 0.035\Omega, \quad X_1 = 0.22\Omega, \quad X_2 = 0.012\Omega$$

$$\therefore K = \frac{E_2}{E_1} = \frac{120}{2400} = 0.05, \quad I_1 = \frac{30 \times 1000}{2400} = 12.5\text{ Amp}, \quad I_2 = \frac{30 \times 1000}{120} = 250\text{ Amp}$$

Equivalent resistance as referred to both primary & secondary.

$$R_{01} = R_1 + \frac{R_2}{K^2} = 0.1 + \frac{0.035}{(0.05)^2} = 14.1\Omega$$

$$R_{02} = K^2 R_{01} = (0.05)^2 \times 14.1 = 0.03525\Omega$$

Equivalent Reactance as referred to both primary & secondary.

$$X_{01} = X_1 + \frac{X_2}{K^2} = 0.22 + \frac{0.012}{(0.05)^2} = 5.02\Omega$$

$$X_{02} = K^2 X_{01} = (0.05)^2 \times 5.02 = 0.0125\Omega$$

Equivalent Impedance as referred to both primary & secondary.

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = 14.1 \Omega \quad \text{and} \quad Z_{02} = \sqrt{R_{02}^2 + X_{02}^2} = 5.02 \Omega$$

Copper loss at full load

$$\therefore W_{Cu} = I_2^2 R_{02} = (250)^2 \times 0.03525 = 2203.25 \text{ watt} = 2.203 \text{ KW}$$

At 75% full load, $x = 0.75$

$$W_{Cu} = x^2 \times W_{CuHL} = 1.2393 \text{ kW}$$

(3) A 5 KVA 200/400 volts, 50Hz single phase transformer gave the following test results.

O.C test [LV side] 200V 0.7A 60W;

S.C test [HV side] 22V 16V 120W

(i) Draw the equivalent circuit of the transformer referred to LV side insert all parameter values.

(ii) Efficiency at 0.9 power factor leading if operating at rated load.

(iii) Currents at which efficiency is maximum, also find load kVA at max. η .

[M-14][6],[Dec-11][10][Dec-10][12]

Solution:-

Given : 5 kVA, 200/400 volt, 50Hz

$$V_1 = 200V, \quad I_0 = 0.7A, \quad \omega_i = 60W$$

$$V_{SC} = 22V, \quad I_2 = 10A, \quad \omega_{SC} = 120W$$

From OC test :

$$\therefore W_1 = V_1 I_0 \cos \phi_0 \Rightarrow \cos \phi_0 = \frac{\omega_i}{V_1 I_0} = \frac{60}{200 \times 0.7} = 0.4285$$

$$\therefore \phi_0 = 64.62^\circ \quad \text{and} \quad \sin \phi_0 = 0.9$$

$$\therefore I_w = I_0 \cos \phi_0 \quad I_w = 0.7 \times 0.4285 = 0.2999 \text{ Amp.}$$

$$\therefore I_\mu = I_0 \sin \phi_0 = 0.7 \times 0.9 = 0.63 \text{ Amp.}$$

$$\therefore R_0 = \frac{V_1}{I_w} = \frac{200}{0.2999} = 666.89 \Omega \quad \text{and} \quad X_0 = \frac{V_1}{I_\mu} = \frac{200}{0.63} = 317.46 \Omega$$


Form SC test:

$$\therefore \omega_{SC} = I_2^2 R_{02} \quad \therefore R_{02} = \frac{\omega_{SC}}{I_2^2} = \frac{120}{16^2} = 0.4687 \Omega$$

$$\therefore Z_{02} = \frac{V_{SC}}{I_2} = \frac{22}{16} = 1.375 \Omega \quad \text{and} \quad X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{(1.375)^2 - (0.4687)^2} = 1.2926 \Omega$$

$$\text{Now, } K = \frac{E_2}{E_1} = \frac{400}{200} = 2$$
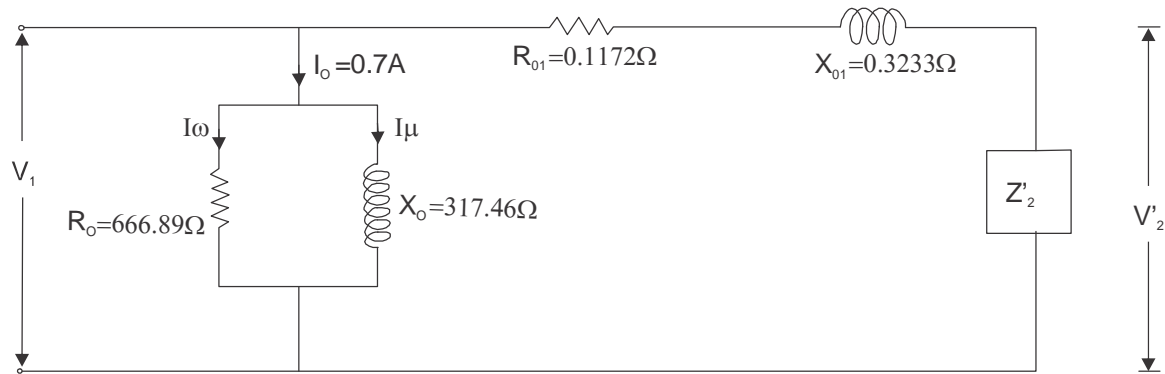
$$\therefore R_{01} = \frac{R_{02}}{K^2} = \frac{0.4687}{2^2} = 0.1172 \Omega \quad \text{and} \quad X_{01} = \frac{X_{02}}{K^2} = \frac{1.2926}{2^2} = 0.3232 \Omega$$



$$(I_2)_{FL} = \frac{\text{kVA rating} \times 1000}{E_2} = \frac{5 \times 1000}{400} = 12.5 \text{ A and } I_2 = 16 \text{ A}$$

$$[W_{Cu}]_{FL} = \left(\frac{12.5}{16} \right)^2 \times 120 = 73.24 \text{ watt}$$

Now pf = 0.9 X = 1....rated load

$$\therefore \% \eta = \frac{X \times \text{full load kVA} \times \text{pf}}{(X \times \text{full load kVA} \times \text{pf}) + \omega_i + X^2 \omega_{Cu}} \times 100 = \frac{1 \times 5 \times 0.9}{(1 \times 5 \times 0.9) + (0.06) + (1)^2 \times 0.07324} \times 100$$

$$\% \eta = 0.9712 \times 100 = 97.12\%$$

$$\therefore \eta = 0.9712$$

- (4) A 50KVA, 4400/220 volt transformer has $R_1 = 3.45\Omega$, $R_2 = 0.009\Omega$. The reactance are $X_1 = 5.2\Omega$ and $X_2 = 0.015\Omega$. Calculate for the transformer,

- Full load currents on primary and secondary side,
- Equivalent resistance, reactances, impedance, referred to primary side and secondary side,
- Total copper lose using individual resistance and equivalent resistances. [M-14][8]

Solution:-

Given : 50kVA, 4400/220 volt transformer i.e.

$$E_1 = 4400 \text{ V}, \quad R_1 = 3.45 \Omega, \quad X_1 = 5.2 \Omega$$

$$E_2 = 220 \text{ V}, \quad R_2 = 0.009 \Omega, \quad X_2 = 0.015 \Omega$$

$$k = \frac{E_2}{E_1} = 0.05$$

$$I_1 = \frac{\text{KVA rating} \times 1000}{E_1} = \frac{50 \times 1000}{4400} = 11.364 \text{ Amp.}$$

$$I_2 = \frac{\text{KVA rating} \times 1000}{220} = 227.273 \text{ Amp}$$

Refer to the primary side

$$\text{Resistance, } R_{01} = R_1 + R_2^1 = R_1 + \frac{R_2}{K^2} = 3.45 + \frac{0.009}{0.05^2}$$

$$\therefore R_{01} = 7.05 \Omega$$

$$\text{Resistance, } X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 5.2 + \frac{0.015}{0.05^2}$$

$$\therefore X_{01} = 11.2 \Omega$$

$$\text{Impedance, } Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = 13.23 \Omega$$

Refer to secondary side,

$$\text{Resistance, } R_{02} = R_2 + R_1' = R_2 + K^2 R_1 = 0.009 + (0.05)^2 \times 3.45 = 0.017625 \Omega$$

$$\text{Resistance, } X_{02} = X_2 + X_1' = X_2 + K^2 X_1 = 0.015 + (0.05)^2 \times 5.2 = 0.028 \Omega$$

$$\text{Impedance, } Z_{02} = \sqrt{R_{02}^2 + X_{02}^2} = 0.033 \Omega$$

Total copper loss,

Using individual resistances,

$$W_{cu} = I_1^2 R_1 + I_2^2 R_2 = 11.364^2 \times 3.45 + 227.273^2 \times 0.009$$

$$W_{cu} = 910.412 \text{ watt}$$

Using equivalent resistance,

$$\text{Using } R_{01}, W_{cu} = I_1^2 R_{01} = 11.364^2 \times 7.05$$

$$W_{cu} = 910.44 \text{ watt}$$

$$\text{Using } R_{02}, W_{cu} = I_2^2 R_{02} = 227.273^2 \times 0.017625$$

$$W_{cu} = 910.38 \text{ watt}$$

- (5) The following results were obtained on a 40 KVA, 2400/120 V transformer.

O.C.Test: 120V, 9.65A and 396W (on L.V. side)

S.C.Test: 92V, 20.8A and 810W (on H.V. side)

Calculate the parameter of approximate equivalent circuit referred to H.V. side. [D-13][6],[May 09][8]

Solution:-

Given: 40 kVA, 2400/120 V transformer

S.C. test is carried out on H.V. side i.e. primary side in given problem

$$\therefore W_{SC1} = 810 \text{ W}, \quad I_1 = 20.8 \text{ A} \quad V_{SC} = 92 \text{ V}$$

$$\therefore W_{SC1} = I_1^2 R_{01} \Rightarrow R_{01} = \frac{W_{SC1}}{I_1^2} = \frac{810}{(20.8)^2} = 1.8722 \Omega$$

$$\therefore Z_{01} = \frac{V_{SC1}}{I_1} = \frac{92}{20.8} = 4.42 \Omega$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = 4 \Omega$$

- (6) A 5kVA, 1000/200 V, 50 Hz, single phase transformer gives following test results:

OC test (LV side) 200V 1.2A 90W

SC test (HV side) 50V 5A 110 W

Determine efficiency as half load at 0.8 p.f. lagging.

[M-13][6]

Solution:-

Given: KVA Rating = 5 KVA, $E_1 = 1000V$, $E_2 = 200V$, $f = 50Hz$

From OC test (LV side i.e. secondary side)

$$W_i = 90W = 0.09 \text{ KW}$$

From SC test (HV side i.e. primary side)

$$W_{sc} = 110W = 0.11KW$$

$$\text{Full load current} = \frac{\text{KVA rating} \times 1000}{E_1} \Rightarrow I_1 = \frac{5 \times 1000}{1000} = 5 \text{ Amp}$$

$$W_{cu} = W_{sc} = 0.11 \text{ kW}$$

Efficiency at half load & 0.8 pf lagging

$$\therefore X = 0.5 \text{ and } pf = 0.8$$

$$\% \eta = \frac{X \times \text{full load KVA} \times pf}{X \times \text{full load KVA} \times pf \times W_i + X^2 W_{cu}} \times 100$$

$$= \frac{0.5 \times 5 \times 0.8}{0.5 \times 5 \times 0.8 + 0.09 + (0.5)^2 \times 0.11} = 94.45$$

- (7) A 230/110V, single phase transformer takes an input of 350 VA at no load and at rated voltage.

The core loss is 110 W. Find (i) The iron loss component of no load current

(ii) magnetizing component of no load current and (iii) No load power factor.

[D-12][6]

Solution:-

$V_1 = 230V$, $V_2 = 110V$, KVA rating = 350 VA

$$(I) W_i = 110W$$

$$W_i = V_1 I_0 \cos \phi_0 \Rightarrow 110 = 230 I_0 \cos \phi_0$$

$$\therefore \text{Iron loss component, } I_w = I_0 \cos \phi_0 = \frac{110}{230} = 0.478A$$

$$(II) \text{ N.L. Input } = 350 \text{ VA} = V_1 I_0 = 230 I_0$$

$$I_0 = 1.521A$$

$$(III) \text{ Now } I_w = I_0 \cos \phi_0 \Rightarrow 0.478 = 1.521 \times \cos \phi_0$$

$$\therefore \text{ N.L.P.F. } = \cos \phi_0 = \frac{0.478}{1.521} = 0.3142 \text{ lagging}$$

(IV) Magnetizing component

$$I_\mu = I_0 \sin \phi_0 = I_0 [\sqrt{1 - \cos^2 \phi_0}] = 1.521 [\sqrt{1 - (0.3142)^2}] = 1.488A$$

- (8) A 5 KVA, 400/200 V, 50 Hz, single phase transformer gave the following results during open and short circuit tests.

O.C. Test : 400V 1A 60 W (H. V. Side)

S.C. Test : 15V 12.5A 50 W (H. V. Side)

Calculate:

- (i) No. load parameters R_0 and X_0 .
- (ii) Equivalent resistance and reactance referred to high voltage side
- (iii) Regulation at full load and 0.8 pf lagging.
- (iv) Iron and copper losses at full load.
- (v) Efficiency at half load and 0.8 pf lagging.

[M-12][10]

Solution:

Given: kVA = 5, $V_1 = 400$ V, $V_2 = 200$ V, $K = 0.5$, $f = 50$ Hz, $V_1 = 400$ V, $I_0 = 1$ A,
 $W_o = 60$ W, $V_{SC} = 15$ V, $I_{SC} = 12.5$ A, $W_{SC} = 50$ W.

It is seen that $I_{SC} = I_1$ rated = 12.5 Amp.

- (i) No load parameters R_0 and X_0 :

From to OC test results,

$$\cos \phi_0 = \frac{W_o}{V_1 I_0} = \frac{60}{400 \times 1} = 0.15 \Rightarrow \phi_0 = 81.37^\circ$$

$$\therefore \sin \phi_0 = 0.9886$$

$$\therefore R_0 = \frac{V_1}{I_0 \cos \phi_0} = \frac{400}{1 \times 0.15} = 2.667 \text{ k}\Omega$$

$$\therefore X_0 = \frac{V_1}{I_0 \sin \phi_0} = \frac{400}{1 \times 0.9886} = 404.61 \Omega$$

- (ii) Equivalent resistance and reactance referred to H.V. side:

From the SC test,

$$R_{IT} = \frac{W_{SC}}{I_{SC}^2} = \frac{50}{(12.5)^2} = 0.32 \Omega$$

$$Z_{IT} = \frac{V_{SC}}{I_{SC}} = \frac{15}{12.5} = 1.2 \Omega$$

$$\therefore X_{IT} = \left(Z_{IT}^2 - R_{IT}^2 \right)^{1/2} = [(1.2)^2 - (0.32)^2]^{1/2} = 1.16 \Omega$$

- (iii) Regulation at full load and 0.8 PF lagging:

$$\cos \phi = 0.8, \quad \therefore \sin \phi = 0.6$$

$$\% \text{ Regulation} = \frac{[I_1 R_{IT} \cos \phi + I_1 X_{IT} \sin \phi]}{V_1} \times 100 = \frac{[(12.5 \times 0.32 \times 0.8) + (12.5 \times 1.16 \times 0.6)]}{400} \times 100$$

$$\therefore \% \text{ Regulation} = 2.975\%$$

- (iv) Iron and copper losses at full load:

$$\text{Iron losses } P_i = W_o = 60 \text{ W}$$

$$\text{Full load current } I_{1(FL)} = \frac{5 \times 10^3}{400} = 12.5 \text{ Amp.}$$

Since $I_{1(FL)} = I_{SC}$, the value of W_{SC} represents the full load copper loss

$$\therefore P_{cu(FL)} = W_{SC} = 50W$$

(v) Efficiency at half load and $\cos \phi = 0.8$:

$$\% \eta_{HL} = \frac{0.5 \times kVA \times 10^3 \times \cos \phi}{(0.5 \times kVA \times 10^3 \times \cos \phi) + P_i + P_{cu(HL)}} \times 100$$

$$\text{But } P_{cu(HL)} = \frac{1}{4} \times P_{cu(FL)} = \frac{1}{4} \times 50 = 12.5W$$

$$\% \eta_{HL} = \frac{0.5 \times 5000 \times 0.8}{(0.5 \times 5000 \times 0.8) + 60 + 12.5} \times 100 = 96.5\%$$

(9) In a 50 KVA, 1100/220 V transformer, the iron and copper losses at full load are 350 W and 425 W respectively. Calculate the efficiency at

- (i) Full load with unity power factor
- (ii) Half load with unity power factor
- (iii) Full load with 0.8 pf lagging.

Also determine the maximum efficiency and the load at which maximum efficiency occurs assuming the load to be resistive. [M-12][10]

Solution:

Given: kVA = 50, $V_1 = 1100$ V, $V_2 = 220$ V, $P_i = 350$ W, $P_{cu(FL)} = 425$ W

(i) Efficiency at full load and $\cos \phi = 1$:

$$\% \eta_{FL} = \frac{kVA \times 10^3 \times \cos \phi}{(kVA \times 10^3 \times \cos \phi) + P_i + P_{cu(FL)}} \times 100 = \frac{50 \times 10^3 \times 1}{(50 \times 10^3 \times 1) + 350 + 425} \times 100$$

$$\therefore \eta_{FL} = 98.47\%$$

(ii) Efficiency at half load and $\cos \phi = 1$:

$$P_{cu(HL)} = \frac{1}{4} \times P_{cu(FL)} = \frac{1}{4} \times 425 = 106.25 W$$

$$\% \eta_{HL} = \frac{0.5 \times KVA \times 10^3 \times \cos \phi}{(0.5 \times kVA \times 10^3 \times \cos \phi) + P_i + P_{cu(HL)}} \times 100 = \frac{0.5 \times 50 \times 10^3 \times 1}{(0.5 \times 50 \times 10^3 \times 1) + 350 + 106.25} \times 100$$

$$\therefore \eta_{HL} = 98.21\%$$

(iii) Efficiency at half load and $\cos \phi = 0.8$:

$$\% \eta_{HL} = \frac{0.5 \times 50 \times 10^3 \times 0.8}{(0.5 \times 50 \times 10^3 \times 0.8) + 350 + 106.25} \times 100$$

$$\therefore \eta_{HL} = 97.77\%$$

- (10) A 100 kVA, 1000/10,000V, 50Hz 1-phase transformer has iron losses of 1100 watts the copper loss with 5A in high voltage winding is 400 watts. Calculate the efficiency at 25% of full load at:

(i) UPF (ii) 0.8 lagging pf, the output being maintained at 10,000 V

[M-11][10]

Solution:

Given: A transformer 100 kVA 100/10,000 Volts, Iron loss $P_i = 1100$ Watts

Copper loss P_{cu} with 5 A at 1000 Volts = 400 Watts

To find: Efficiency at 25% load at (a) unity p.f. (b) 0.8 p.f. lagging

Step 1: Find current at 25% load:

Output at 25% load = 25 kVA

$$\text{corresponding current} = \frac{25 \times 1000}{10000} = 2.5 \text{ A}$$

Step 2: Find current loss and total loss at 2.5 Amp:

$$\therefore \text{Current loss} = 400 \times \left(\frac{2.5}{5}\right)^2 = 100 \text{ Watt}$$

$$\therefore \text{Total loss} = 1100 + 100 = 1200 \text{ Watt} = 1.2 \text{ kW}$$

Step 3: Find output at 25% load unity pf and efficiency:

$$\text{Output at 25\% load unity pf} = 25 \times 1 = 25 \text{ kW}$$

$$\therefore \eta \text{ at 25\% load unity pf} = \frac{\text{output}}{\text{output} \times \text{Losses}} \times 100 = \frac{25}{25 + 1.2} = \frac{25}{26.2} \times 100$$

$$\therefore \eta \text{ at 25\% load unity pf} = 95.42\%$$

Step 4: Find output at 25% load 0.8 p.f. lagging and efficiency:

$$\text{Output} = 25 \times 0.8 = 20 \text{ kW}$$

$$\therefore \eta \text{ at 25\% load unity pf} = \frac{\text{output}}{\text{output} \times \text{Losses}} \times 100 = \frac{20}{20 + 1.2} \times 100 = \frac{20}{21.2} \times 100$$

$$\therefore \eta \text{ at 25\% load unity pf} = 94.34\%$$

- (11) Obtain the equivalent circuit of a 200/400 volts 50 Hz single phase transformer from the following tests. O.C. test : 200V 0.7A 70 W on L. V. side

S.C. test : 15V 10A 85 W on H. V. side

Calculate the secondary voltage when delivering 5 kw, 0.8 p.f. lagging the primary voltage being 200V.

[Dec 09][10]

Solution:-

Given : $V_{oc} = 200\text{V}$, $I_0 = 0.7 \text{ A}$, $W_0 = 70\text{W}$, $V_{sc} = 15 \text{ V}$, $I_{sc} = 10\text{A}$, $W_{sc} = 85 \text{ W}$, $V_1/V_2 = 200/400$

To Find : Equivalent circuit , Secondary voltage for $P_2 = 5 \text{ kW}$, $\cos \phi_2 = 0.8$ and $V_1 = 200 \text{ V}$.

Part I : Equivalent Circuit

Step 1 : Find $R_0, X_0, R_{2T}, X_{2T}, R_1, R_{1T}$

$$\text{From the O.C test, } \cos \phi_o = \frac{W_0}{V_{oc} I_0} = \frac{70}{200 \times 0.7} = 0.5 \quad \therefore \phi = 60^\circ$$

$$\therefore \sin \phi_o = 0.866$$

$$\therefore R_o = \frac{V_{oc}}{I_o \cos \phi_o} = \frac{200}{0.7 \times 0.5} = 571.43 \Omega$$

$$\therefore X_o = \frac{V_{oc}}{I_o \sin \phi_o} = \frac{200}{0.7 \times 0.866} = 329.92 \Omega$$

From the S.C test $W_{sc} = I_{sc}^2 \times R_{2T}$

$$\therefore R_{2T} = \frac{W_{sc}}{I_{sc}^2} = \frac{85}{(10)^2} = 0.85 \Omega \quad \text{and} \quad Z_{2T} = \frac{V_{sc}}{I_{sc}} = \frac{15}{10} = 1.5 \Omega$$


$$\therefore X_{2T} = \sqrt{Z_{2T}^2 - R_{2T}^2} = \sqrt{(1.5)^2 - (0.85)^2} = 1.24 \Omega$$

Transformation ratio $k = \frac{V_2}{V_1} = \frac{400}{200} = 2$

$$\therefore R_{1T} = \frac{R_{2T}}{k^2} = \frac{0.85}{4} = 0.2125 \Omega \quad \text{and} \quad \therefore X_{1T} = \frac{X_{2T}}{k^2} = \frac{1.24}{4} = 0.31 \Omega$$

Step 2 : Draw the equivalent circuit :

The equivalent circuit with respect to the primary (low voltage) winding is as shown in fig 9.

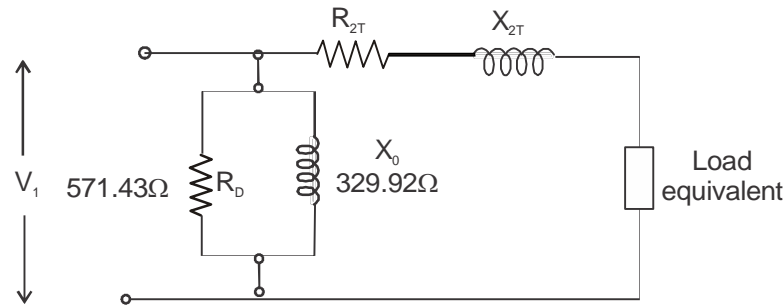

Part II : Secondary Voltage

Given : $V_1 = 200 \text{ V}$, $\cos \phi_2 = 0.8$, $P_2 = 5 \text{ kW}$

The secondary induced voltage $E_2 = kV_1 = 2 \times 200 = 400 \text{ V}$

$$P_2 = E_2 I_2 \cos \phi_2$$

$$\therefore I_2 = \frac{5 \times 10^3}{400 \times 0.8} = 15.625 \text{ Amp}$$

$$\therefore \text{Load voltage } V_2 = E_2 - I_2 [R_{2T} \cos \phi_2 + X_{2T} \sin \phi_2]$$

$$\cos \phi_2 = 0.8, \quad \therefore \phi = 36.87^\circ \quad \therefore \sin \phi = 0.6$$

$$\therefore V_2 = 400 - 15.625 [0.85 \times 0.8 + 1.24 \times 0.6]$$

$$\therefore V_2 = 399 \text{ volts}$$

(12) A 20 KVA, 2000/200 V, transformer has primary resistance and reactance of 2.3Ω and 4.2Ω respectively. Corresponding secondary values are 0.025Ω and 0.04Ω . Open circuit loss is 200 watts. Determine-

- (i) Equivalent resistance and reactance referred to primary and secondary
- (ii) Full load regulation and efficiency at 0.8 power factor lagging.

[M-08][8]

Solution :

Given:- kVL = 20, $V_1 = 2000\text{V}$, $W_O = 200\text{W}$, $R_1 = 2.3 \Omega$, $R_2 = 0.025 \Omega$, $X = 0.04 \Omega$

To find:- R_{1T} , X_{1T} , R_{2T} , X_{2T} , η_{FL} , % R

Equivalent resistances and reactance:

$$K = \frac{V_2}{V_1} = 200 / 2000 = 0.1$$

R_{1T} and X_{1T} (primary) :

$$R_{1T} = R_1 + \frac{R_2}{K^2} = 2.3 + \frac{(0.025)}{(0.1)^2} = 4.8 \Omega \quad \text{and} \quad X_{1T} = X_1 + \frac{X_2}{K^2} = 4.2 + \frac{(0.04)}{(0.1)^2} = 8.2 \Omega$$

R_{2T} and X_{2T} (secondary) :

$$R_{2T} = R_2 + K^2 R_1 = 0.025 + (0.1)^2 \times 2.3 = 0.048 \Omega$$

$$X_{2T} = X_2 + K^2 X_1 = 0.04 + (0.1)^2 \times 4.2 = 0.082 \Omega$$

Full load efficiency :

$$\text{Full load secondary current } I_{2(FL)} = \frac{V_A}{V_2} = \frac{20 \times 10^3}{200} = 100 \text{ A}$$

$$\therefore \text{ Full load copper loss } P_{cu(FL)} = I_{2(FL)}^2 \times R_{2T} = 100^2 \times 0.048 = 480 \text{ W}$$

$$\therefore \text{ Iron loss} = 200 \text{ W}$$

$$\eta_{FL} = \frac{\text{kVA} \times 1000 \times \cos \phi}{\text{kVA} \times 1000 \times \cos \phi + P_i + P_{cu(FL)}} = \frac{20 \times 1000 \times 0.8}{(20 \times 1000 \times 0.8) + 200 + 480}$$

$$\therefore \eta_{FL} = 0.9592 \text{ or } 95.92\%$$

Regulation :

$$V_{2(FL)} = 200\text{V}$$

$$E_2 = V_2 + I_{2FL} [R_{2T} \cos \phi + X_{2T} \sin \phi]$$

$$\text{But } \cos \phi = 0.8 \quad \sin \phi = 0.6$$

$$\therefore E_2 = 200 + 100 [(0.048 \times 0.8) + (0.082 \times 0.6)] = 208.76 \text{ V}$$

$$\begin{aligned} \text{Percentage Regulation} &= \frac{E_2 - E_1}{E_2} \times 100 = \frac{208.76 - 200}{208.76} \times 100 \\ &= 4.196\% \end{aligned}$$

- (13) Calculate the (a) Full load efficiency at 0.8 p.f. (lag) (b) Terminal voltage when supplying full load at 0.8 p.f. (lag) for an input voltage of 500V. The result of O.C. and S.C. test on 5 KVA, 500/250 V, 50 Hz, 1- ϕ transformer are as follows: [D-07][8]

$$\begin{array}{llll} \text{O.C. :} & 500\text{V} & 1\text{A} & 50\text{W} \\ \text{S.C. :} & 15\text{V} & 6\text{A} & 21.6\text{W} \end{array}$$

Solution :

Given : $V_{SC} = 15\text{V}$, $I_{SC} = 6\text{A}$, $W_{SC} = 21.6\text{W}$, $V_O = 500\text{ V}$, $I_O = 1\text{A}$, $W_O = 50\text{ W}$
 Form S.C test find R_{2T} , X_{2T} , and Z_{2T} :

$$Z_{2T} = \frac{V_{SC}}{I_{SC}} = 15 / 6 = 2.5\Omega \quad \left(\text{But } W_{SC} = I_{SC}^2 \times R_{2T} \right)$$

$$\therefore R_{2T} = \frac{W_{SC}}{I_{SC}^2} = \frac{21.6}{6^2} = 0.6\Omega$$

$$\therefore X_{2T} = \sqrt{Z_{2T}^2 - R_{2T}^2} = \sqrt{(2.5)^2 - (0.6)^2} = 2.43\Omega$$

Calculate full load copper and iron loss :

$$I_{2(PL)} = VA / V_2 = (5 \times 1000) / 250 = 20\text{A}$$

$$P_{cu} = W_{SC} \text{ at } 6\text{A} = 21.6\text{ W at } 6\text{A}$$

$$\therefore P_{cu} \text{ at } 6\text{A} = \left(\frac{6}{20} \right)^2 \times P_{cu}$$

$$P_{cu(FL)} = \left(\frac{20}{6} \right)^2 \times P_{cu} \text{ at } 6\text{A} = \left(\frac{6}{20} \right)^2 \times 21.6$$

$$\therefore P_{cu(FL)} = 240\text{ W}$$

Iron loss $P_i = W_O = 50\text{ W}$ from O.C test

Calculate η at F.L.:

$$\begin{aligned} \eta_{FL} &= \frac{kVA \times 1000 \times P.f}{(kVA \times 1000 \times P.f) + [P_i + P_{cu(FL)}]} = \frac{5 \times 1000 \times 0.8}{(5 \times 1000 \times 0.8) + [50 + 240]} \\ &= 0.9324 \text{ or } (93.24\%) \end{aligned}$$

Terminal voltage :

$$\cos \phi = 0.8 \Rightarrow \phi = 36.87^\circ \Rightarrow \sin \phi = 0.6$$

$$\begin{aligned} \therefore \text{Terminal voltage} &= E_2 - I_{2FL} [R_{2T} \cos \phi + X_{2T} \sin \phi] \\ &= 250 - 20 [(0.6 \times 0.8) + (2.43 \times 0.6)] = 211.24\text{ V} \end{aligned}$$

- (14) A transformer has its maximum efficiency of 98% at 15 kVA at UPF. During the day it is loaded as follows:
- | | |
|----------|-------------------|
| 12 hrs : | 2 kW at 0.5 p.f. |
| 6 hrs : | 12 kW at 0.8 p.f. |
| 6 hrs : | 18 kW at 0.9 p.f. |

Find the all-day efficiency.

[D-07][8]

Solution:-

Step 1: To find the Iron and full load copper loss :

$$\eta_{\max} = \frac{\text{kVA} \times 10^3 \times \text{PF}}{(\text{kVA} \times 10^3 \times \text{PF}) + P_i + P_{\text{cu}}}$$

$$\text{But } P_i = P_{\text{cu}} \text{ (for } \eta_{\max}) \Rightarrow P_i + P_{\text{cu}} = 2P_i$$

$$\therefore 0.98 = \frac{15 \times 10^3 \times 1}{(15 \times 10^3 \times 1) + 2P_i} \Rightarrow P_i = 153 \text{ W}$$

$$\text{Assuming kVA full load} = \frac{18}{0.9} = 20 \text{ kVA from the given data}$$

$$\therefore \text{ kVA for maximum efficiency} = \text{Full load kVA} \sqrt{\frac{\text{Iron loss}}{\text{Full load copper loss}}}$$

$$\therefore 15 \text{ kVA} = 20 \text{ kVA} \sqrt{\frac{0.153 \text{ kW}}{P_{\text{cu(FL)}}}}$$

$$\therefore P_{\text{cu(FL)}} = 0.272 \text{ kW or } 272 \text{ W}$$

Step 2 : To calculate total loss :

$$P_{\text{cu}} \text{ at full load (20 kVA)} = 272 \text{ W}$$

$$P_{\text{cu}} \text{ at 15 kVA} = 153 \text{ W}$$

$$P_{\text{cu}} \text{ at 4 kVA} = \left(\frac{4}{20}\right)^2 \times 272 = 10.88 \text{ W}$$

$$\therefore \text{Total Cu loss} = (272 \text{ W} \times 6 \text{ h}) + (153 \text{ W} \times 6 \text{ h}) + (10.88 \text{ W} \times 12 \text{ h}) = 2680.56 \text{ Wh}$$

$$\text{Total iron loss} = 153 \text{ W} \times 24 \text{ h} = 3672 \text{ Wh}$$

$$\therefore \text{Total loss} = 2680.56 + 3672 = 6352.56 \text{ Wh}$$

Step 3 : To calculate energy output :

$$\text{Output} = (2 \text{ kW} \times 12 \text{ h}) + (12 \text{ kW} \times 6 \text{ h}) + (18 \text{ kW} \times 6 \text{ h}) = 204 \text{ kWh}$$

Step 4 : All day efficiency :

$$\eta_{\text{all day}} = \frac{\text{Output}}{\text{Output} + \text{loss}} = \frac{204 \times 10^3}{(204 \times 10^3 + 6352.56)} = 0.9698 \text{ or } 96.98 \%$$



ACADEMY

SET TIME SET TARGET

Diploma & Degree Engineering Classes

Crash Course for Degree Engineering

Semester I

1. Applied Maths I
2. Engg Mechanics
3. BEE
4. Applied Physics I



Semester II

1. Applied Maths II
2. Engg Drawing
3. SPA
4. Applied Physics II



Hurry Up!!! Batches Starting from 10th Nov 2016.

Fees: Rs. 4000/Subject

**Passing Guaranteed
or else Refund***

Duration: 10-12 Days, 3 Hours/Day Location: Thane.

Highlights

- ☀ Experienced faculties
- ☀ Modern teaching techniques
- ☀ Batch of limited students
- ☀ Extensive study material
- ☀ Strategies for time saving
- ☀ Individual doubts solving

For Syllabus, QP & Solutions :
www.setsquareacademy.com



**Address : 2nd floor, Govind Smruti, Near Karnavat Classes,
Lohar Ali, Thane (W). 400 602.**

For further details please Call or What'sapp : 9920848746



ACADEMY

SET TIME SET TARGET

Diploma & Degree Engineering Classes

Regular Batches Degree Sem II

Subjects Offered:

1. Applied Mathematics II
2. Engineering Drawing
3. Auto CAD (with Certification)
4. Applied Physics II
5. Structured Programming Approach
6. 'C' Programming (with Certification)

Fees: Only Rs. 7000/-
Per Subject



Batches starting from 7th Jan 2017.

Location : Thane, Vashi & Dombivli.

Special 3D Models for
Engineering Drawing

Highlights

- ☀ Experienced faculties
- ☀ Modern teaching techniques
- ☀ Batch of limited students
- ☀ Extensive study material
- ☀ Strategies for time saving
- ☀ Individual doubts solving

For Syllabus, QP & Solutions :
www.setsquareacademy.com



Address : 2nd floor, Govind Smruti, Near Karnavat Classes,
Lohar Ali, Thane (W). 400 602.

For further details please Call or What'sapp : 9920848746